## ΓΙΩΡΓΟΣ ΧΑΤΖΗΛΙΓΟΣ ΑΜ4835 2° ΕΤΟΣ

 $F(a,b,c,d)=\Sigma(0,1,2,4,5,6,8,10)$ 

Χρησιμοποιω πινακα Karnaugh


AB\CD	0	1	11	10	
0	1	1	0	1	
1	1	1	0	1	
11	0	0	0	0	
10	1	0	0	1	


F=a'b'c'd'+a'b'c'd+a'b'cd'+a'bc'd'+a'bc'd+a'bcd'+ab'cd'=

=a'b'c'(d+d')+a'cd'(b+b')+a'bc'(d+d')+ab'd'(c+c')

=a'c'(b+b')+a'cd'+ab'd'=a'c'+a'cd'+ab'd'

а	b	С	d	a'c'	a'cd'	ab'd'	f
0	0	0	0	1	0	0	1
1	0	0	0	0	0	1	1
0	1	0	0	1	1	0	1
0	0	1	0	1	1	0	1
0	0	0	1	1	0	0	1
1	1	0	0	0	0	0	0
1	0	1	0	0	0	1	1
1	0	0	1	0	0	0	0
0	1	1	0	0	1	0	1
0	1	0	1	1	0	0	1
0	0	1	1	0	0	0	0
1	1	1	0	0	0	0	0
1	0	1	1	0	0	0	0
1	1	0	1	0	0	0	0
1	1	1	1	0	0	0	0

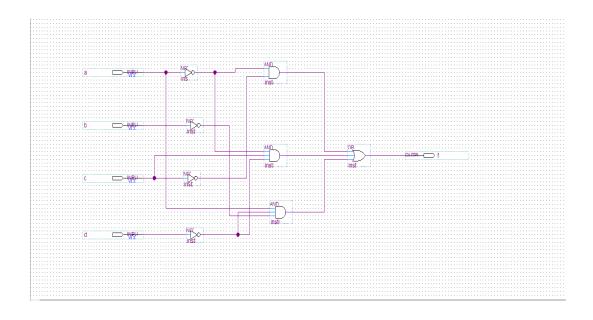

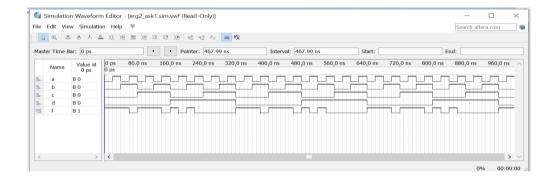

### ΑΣΚΣΗΣΗ 2:

F=xy +xz+ yz


## ΠΙΝΑΚΑΣ ΑΛΗΘΕΙΑΣ


Х	у	Z	f
0	0	0	0
0	0	1	0
0	1	0	0
1	0	0	0
1	1	0	0
1	0	1	1
0	1	1	1
1	1	1	1


## ΠΙΝΑΚΑΣ KARNAUGH

x∖yz	0	1	11	10
0	0	0	1	0
1	0	1	1	1

ΟΠΟΤΕ  $f(x,y,z)=\Sigma(3,5,6,7)$ 

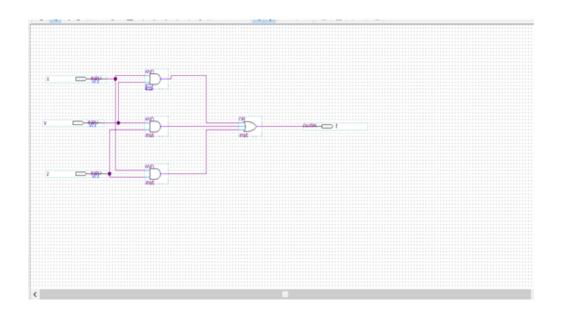

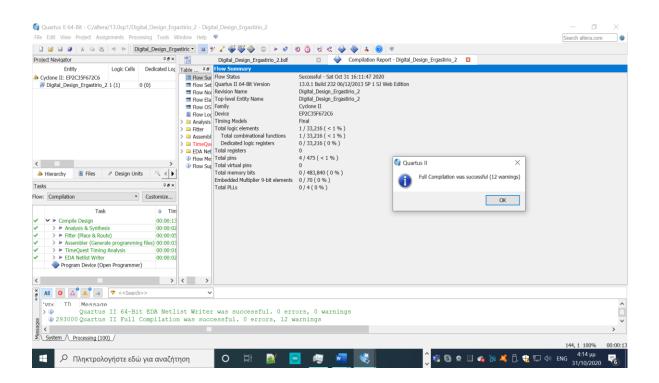

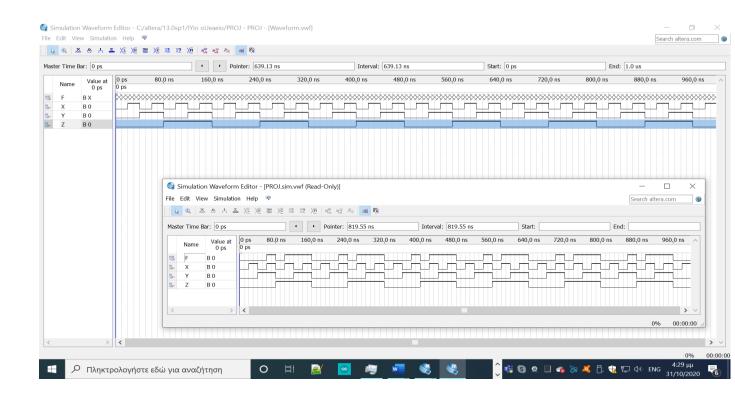

#### ΑΣΚΗΣΗ 3

## F=AB+CD ΠΙΝΑΚΑΣ ΑΛΗΘΕΙΑΣ

а	b	С	d	ab	cd	ab+cd
p0	0	0	0	0	0	0
1	0	0	0	0	0	0
0	1	0	0	0	0	0
0	0	1	0	0	0	0
0	0	0	1	0	0	0
1	1	0	0	1	0	1
1	0	1	0	0	0	0
1	0	0	1	0	0	0
0	1	1	0	0	0	0
0	1	0	1	0	0	0

0	0	1	1	0	1	1
1	1	1	0	1	0	1
1	1	0	1	1	0	1
1	0	1	1	0	1	1
0	1	1	1	0	1	1
1	1	1	1	1	1	1

 $F(A,B,C,D)=\Sigma(3,7,11,12,13,14,15)$ 

# Πινακας Karnaugh:

ab\cd	0	1	11	10
0	0	0	1	0
1	0	0	1	0
11	1	1	1	1
10	0	0	1	0


Για να σχηματισω πυλες nand πρεπει:


 $F = ab + cd = ((ab)')' + ((cd)')' \kappa \alpha \iota \ f' = \{ [(ab)'(cd)']'\}' \ F' = \Sigma(0,1,2,4,5,6,8,9,10,16)$ 

Από deMorgan ((ab)'(cd)')' Ετσι σχηματισα τις πυλες nand


## Πινακας αληθειας

								CI
							f	f'
а	b	С	d	ab	cd	(ab)'(cd)'	[(ab)(cd)]'	{[(ab)(cd)']'}'
0	0	0	0	0	0	1	0	1
1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	1	0	1
0	0	1	0	0	0	1	0	1
0	0	0	1	0	0	1	0	1
1	1	0	0	1	0	0	1	0
1	0	1	0	0	0	1	0	1
1	0	0	1	0	0	1	0	1
0	1	1	0	0	0	1	0	1
0	1	0	1	0	0	1	0	1
0	0	1	1	0	1	0	1	0
1	1	1	0	1	0	0	1	0
1	1	0	1	1	0	0	1	0
1	0	1	1	0	1	0	1	0
0	1	1	1	0	1	0	1	0
1	1	1	1	1	1	0	1	0

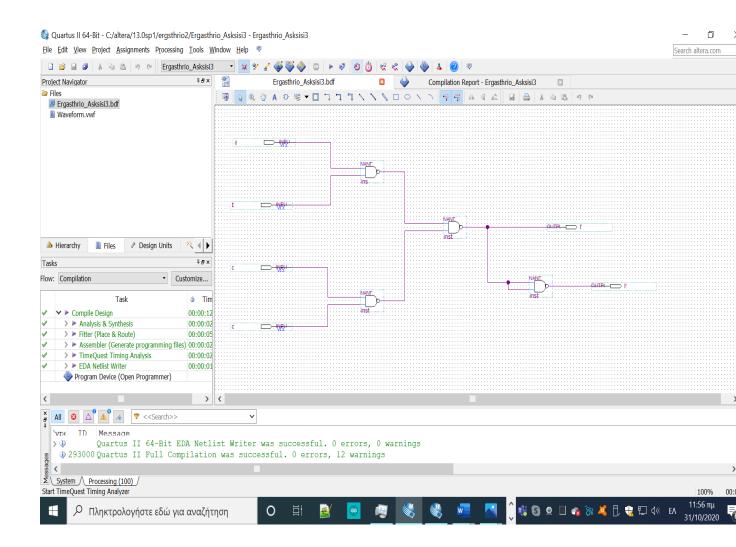

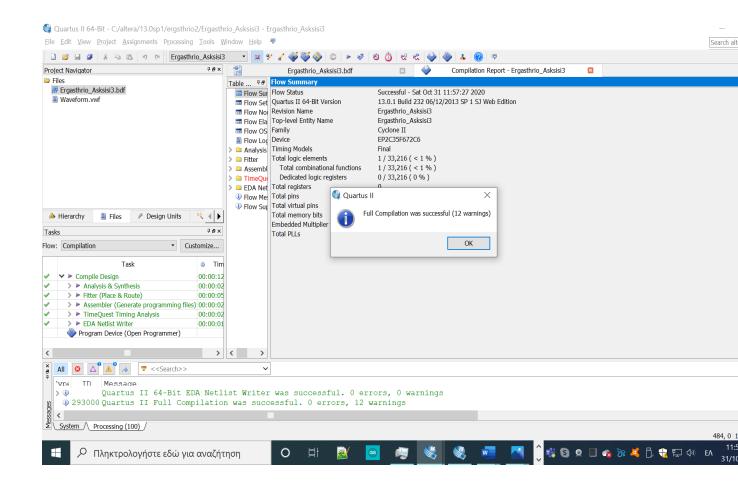

#### \*TO h FINAL TO f'

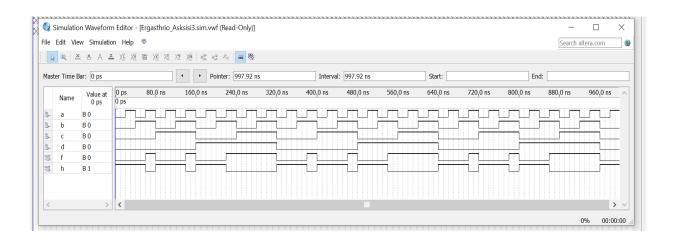

Η F από το προηγουμενο ερωτημα είναι f=((ab)'(cd)')' [(a'+b')(c'+d')]'=(a'c'+a'd'+b'c'+b'd')'=[(a+c)'+(a+d)'+(b+c)'+(b+d)']' Η  $f'=\{[(a+c)'+(a+d)'+(b+c)'+(b+d)']'\}'$ 

Οποτε κατασκευασαμε το κυκλωμα μας μονο με πυλες nor

