

Ασκ 1 Εργαστήριο (3)

Οι 4 εισοδοί μας είναι α, β, γ, δ

				Μετατροπή				
α	β	γ	δ	→	x	y	z	w
0	0	0	0	Διαδικασία σε Gray	0	0	0	0
0	0	0	1		0	0	0	1
0	0	1	0		0	0	1	1
0	0	1	1		0	0	1	0
0	1	0	0		0	1	1	0
0	1	0	1		0	1	1	1
0	1	1	0		0	1	0	1
0	1	1	1		0	1	0	0
1	0	0	0		1	1	0	0
1	0	0	1		1	1	0	1
1	0	1	0		1	1	1	1
1	0	1	1		1	1	1	0
1	1	0	0		1	0	1	0
1	1	0	1		1	0	1	1
1	1	1	0		1	0	0	1
1	1	1	1		1	0	0	0

$\begin{array}{|c|c|c|c|} \hline 1 & 1 & 0 & 0 \\ \hline 1 & 1 & 0 & 1 \\ \hline 1 & 1 & 1 & 0 \\ \hline 1 & 1 & 1 & 1 \\ \hline \end{array}$
 $\begin{array}{|c|c|c|c|} \hline 1 & 0 & 1 & 0 \\ \hline 1 & 0 & 1 & 1 \\ \hline 1 & 0 & 0 & 1 \\ \hline 1 & 0 & 0 & 0 \\ \hline \end{array}$

Όπως δείχνουν οι πίνακες κρατάμε το α συνεχώς ίδιο
 δηλαδή $a=x$ στην μετατροπή μας.
 Απλοποιώ την λύση στο μινιμάλ χρησιμοποιώντας μόνο
 δυο εισόδους και δυο εξόδους

a, b x, y

Εφόσον $a=x$ το y είναι
 αυτό που μας ενδιαφέρει

$\begin{array}{|c|c|c|} \hline a & 0 & 1 \\ \hline b & 0 & 1 \\ \hline 0 & 0 & 1 \\ \hline 1 & 1 & 0 \\ \hline \end{array}$
 $a'b' + a'b = a \oplus b'$


Με πύλη **XOR**

© NEXT Co. GREECE

REDMI NOTE 9S
 AI QUAD CAMERA

Θα δουλέψω το κυκλώμα μου μόνο με πύλες xor:

Ακολουθεί το κυκλώμα :

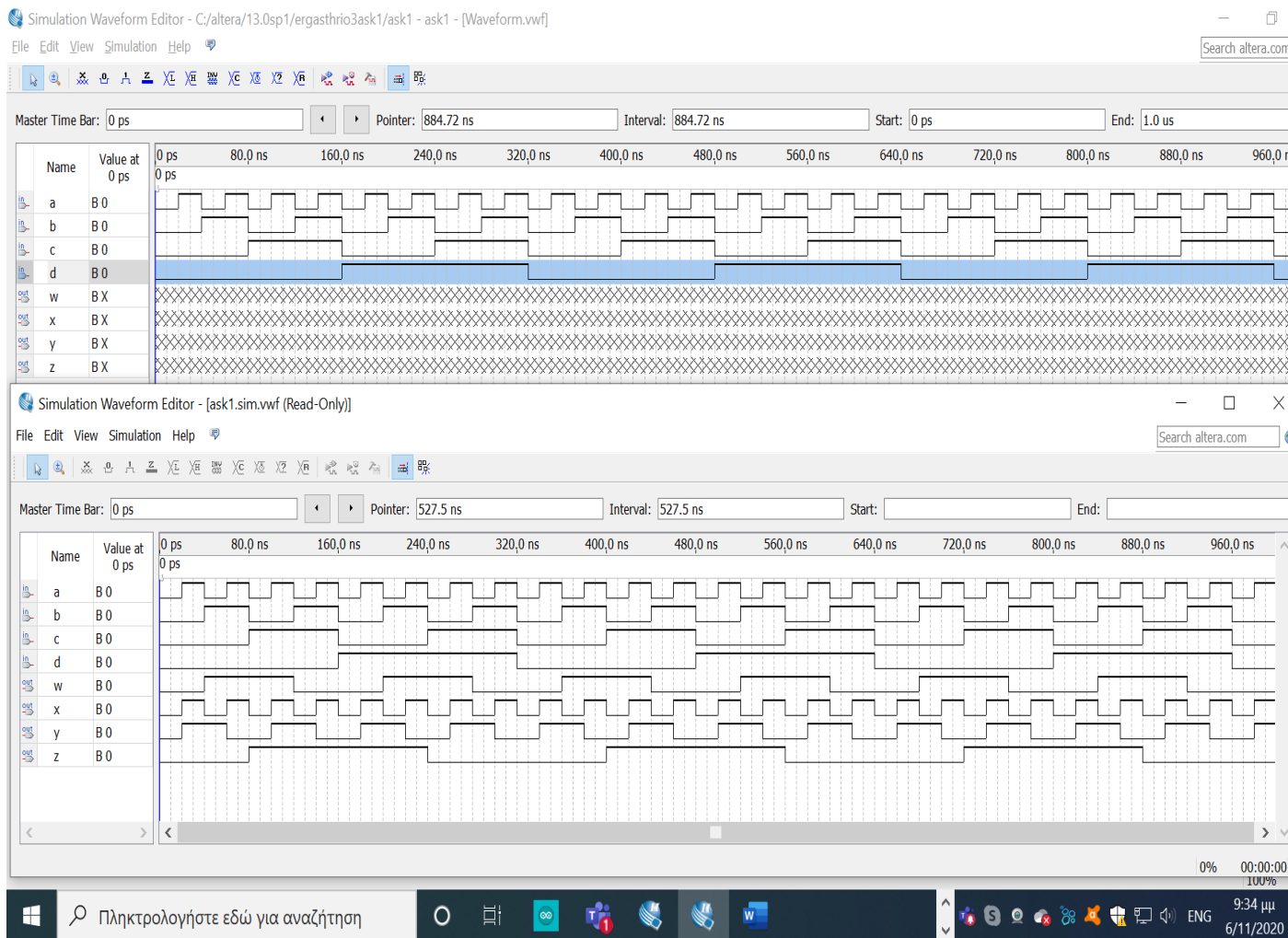

Ακολουθεί Ασκήση2:

Ηολων (2) Εργαστηριο (3)

a	b	c	d	Παρατηρη	w	x	y	z
0	0	0	0	Συμπληρωμα	1	0	0	1
0	0	0	1	ως προς g	1	0	0	0
0	0	1	0	$g = 1010$	0	1	1	1
0	0	1	1	$wxyz = (abcd)' + g$	0	1	1	0
0	1	0	0		0	1	0	1
0	1	0	1		0	1	0	0
0	1	1	0		0	0	1	1
0	1	1	1		0	0	1	0
1	0	0	0		0	0	0	1
1	0	0	1		0	0	0	0

Για το w ωστε να το απλοποιήσω χρησιμοποιώ Karnaugh

ab \ cd	00	01	11	10
00	1	1	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

$$w = a'b'c'd' + a'b'cd = a'b'c'(d' + d) = a'b'c'$$

Για το x

ab \ cd	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	0	0	0	0
10	0	0	0	0

$$x = b \oplus c$$

Διότι,

$$x = a'b'c'd' + a'b'cd + a'b'cd + a'b'cd' = a'b'c'(d' + d) + a'b'c(d + d') = a'b'c' + a'b'c = bc' + b'c = b \oplus c$$

Για τον $y_{ab'cd}$

	0	0	1	1
	0	0	1	1
a	0	0	0	0
	0	0	0	0

$$y = cd'b' + cd'b + cdb + cd'b =$$

$$= cb'(d'+d) + cb(d+d') = cb' + cb = c(b+b') = c$$

$$\boxed{y=c}$$

Οπότε, για το τελευταίο z δεν χρειαζόμαστε
Karnaugh από παρατηρώ από τον πίνακα αληθείας
το είχα ως $\boxed{z=d'}$

- Για να συγχρονίσουμε το ρολόι στον πίνακα αληθείας θα πρέπει να δούμε σε ποια περίπτωση ο πίνακας BCD είναι μεγαλύτερος του 1001. Αρκεί να κάνουμε ένα κυκλωμα. Αν οι εισες του a και b και c είναι ταυτόχρονα 1. Αρα, $\text{fault} = a + (b \cdot c)$

Quartus II 64-Bit - C:/altera/13.0sp1/ergasthrio3_ask2/ergasthrio3_ask2 - ergasthrio3_ask2

File Edit View Project Assignments Processing Tools Window Help

ergasthrio3_ask2

Project Navigator

Entity

- Cyclone II: EP2C35F672C6
- ergasthrio3_ask2

Hierarchy Files Design Units

Tasks

Flow: Compilation Customize...

	Task	Time
✓	Compile Design	00:00:11
✓	Analysis & Synthesis	00:00:01
✓	Fitter (Place & Route)	00:00:05
✓	Assembler (Generate programming files)	00:00:03
✓	TimeQuest Timing Analysis	00:00:01
✓	EDA Netlist Writer	00:00:01
	Program Device (Open Programmer)	

ergasthrio3_ask2.bdf

Compilation Report - ergasthrio3_ask2

Messages

System (2) Processing (100)

Message

Quartus II 64-Bit EDA Netlist Writer was successful. 0 errors, 0 warnings

293000 Quartus II Full Compilation was successful. 0 errors, 12 warnings

Πληκτρολογήστε εδώ για αναζήτηση



ergasthrio3_ask2

Entity

Cyclone II: EP2C35F672C6

ergasthrio3_ask2

ergasthrio3_ask2.bdf

Compilation Report - ergasthrio3_ask2

Table ...

Flow Summary

Flow Status

Successful - Fri Nov 06 23:51:20 2020

Flow Set

Quartus II 64-Bit Version

13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition

Flow Name

Revision Name

ergasthrio3_ask2

Flow Elaboration

Top-level Entity Name

ergasthrio3_ask2

Flow OS

Family

Cyclone II

Flow Logic

Device

EP2C35F672C6

Analysis

Timing Models

Final

Fitter

Total logic elements

3 / 33,216 (< 1 %)

Assembler

Total combinational functions

3 / 33,216 (< 1 %)

TimeQuest

Dedicated logic registers

0 / 33,216 (0 %)

EDA Netlist

Total registers

0

Flow Messages

Total pins

9 / 475 (2 %)

Flow Summary

Total virtual pins

0

Total memory bits

0 / 483,840 (0 %)

Embedded Multiplier 9-bit elements

0 / 70 (0 %)

Total PLLs

0 / 4 (0 %)

Tasks

Flow: Compilation

Customize...

Task	Time
Compile Design	00:00:11
Analysis & Synthesis	00:00:01
Fitter (Place & Route)	00:00:05
Assembler (Generate programming files)	00:00:03
TimeQuest Timing Analysis	00:00:01
EDA Netlist Writer	00:00:01
Program Device (Open Programmer)	

All


TD

Message

Quartus II 64-Bit EDA Netlist Writer was successful. 0 errors, 0 warnings

293000 Quartus II Full Compilation was successful. 0 errors, 12 warnings

System (2) / Processing (100) /

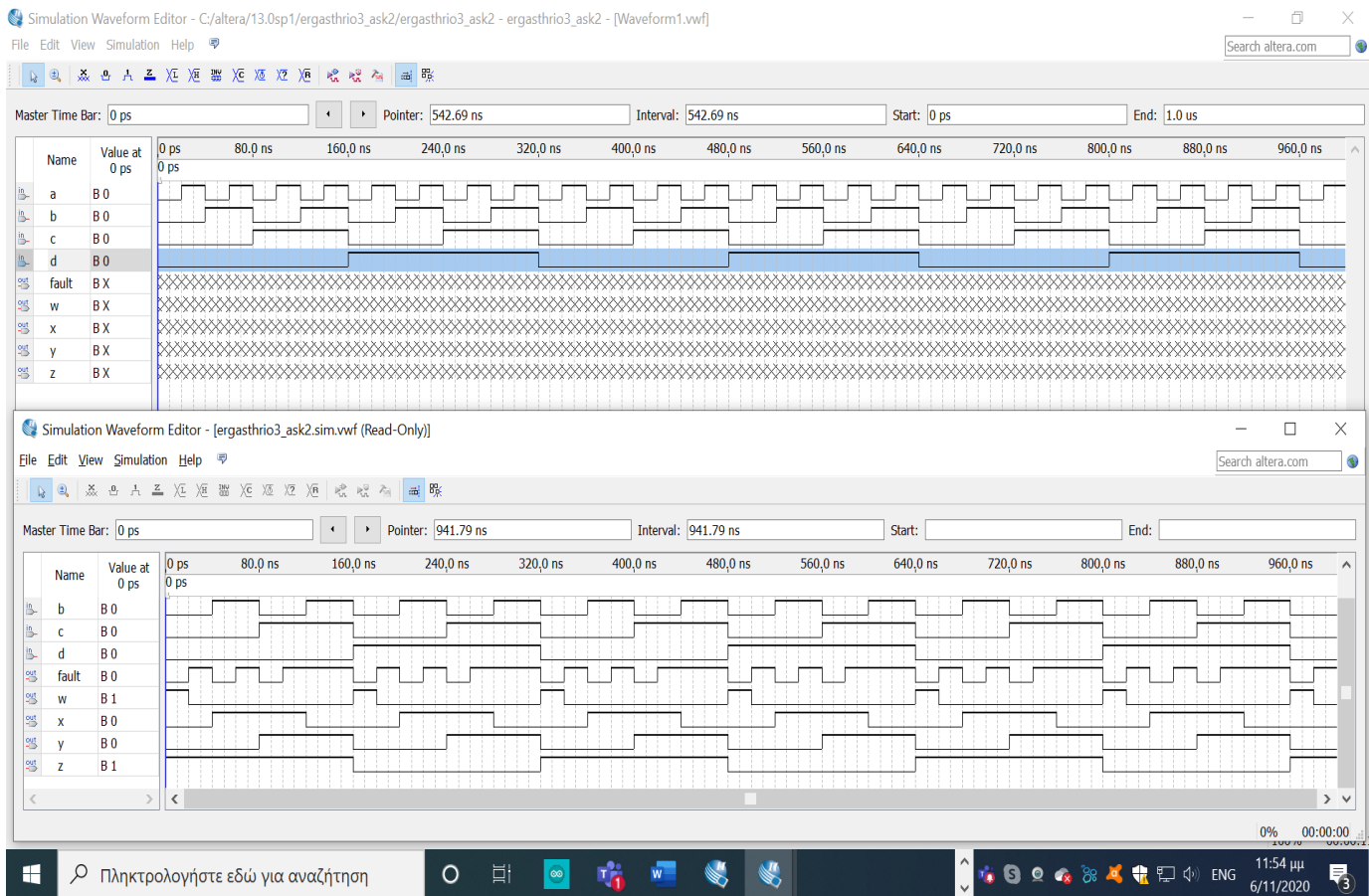

Ακολουθει ασκηση 3:

Ερώτηση (3^η)

Αφού το X έχει 3 ευρεθείς
Επομένως φτάνει μέχρι το 3

x	-4	-3	-2	-1	0	1	2	3
y	10	3	-2	-5	-6	-5	-2	-3

Αρα χρειαζόμαστε 4 εφάκτες για οπότεους
1 για πρόσθετο

~~100~~

c	b	a	\longrightarrow	y_5	y_4	y_3	y_2	y_1
1	0	0	Συμπληρωμα	0	1	0	1	0
1	0	1	ως προς 2	0	0	0	1	1
1	1	0		1	1	1	1	0
1	1	1		1	1	0	1	1
0	0	0		1	1	0	1	0
0	0	1		1	1	0	1	1
0	1	0		1	1	1	1	0
0	1	1		0	0	0	1	1

$f(a, y_1)$	$a \backslash y_1$	00	01	11	10
0	0	0	1	1	0
1	0	1	1	1	0

$y_1 = a$

$f(a, y_2)$	$a \backslash y_2$	00	01	11	10
0	0	1	1	1	1
1	0	1	1	1	1

$y_2 = 1$

1a	y ₃	00	01	11	10
----	----------------	----	----	----	----

0	0	0	0
1	0	0	0

$$y_3 = c' b$$

12	11	10	09	08	07	06	05	04	03	02	01	00
12	11	10	09	08	07	06	05	04	03	02	01	00

0	1	1	0	1
1	0	0	1	1

$$y_9 = c'b' + a' + cb$$

$x \backslash y$	00	01	11	10
0	1	1	0	1
1	0	0	1	1

$$y_3 = c'b' + cb + c'a'$$

Quartus II 64-Bit - C:/altera/13.0sp1/ergasthrio3ask3/ergasthrio3ask3 - ergasthrio3ask3

File Edit View Project Assignments Processing Tools Window Help

ergasthrio3ask3

Project Navigator

Entity	Logic Cells	Dedicated Logic F
Cyclone II: EP2C35F672C6		
ergasthrio3ask3	3 (3)	0 (0)

Tasks

Flow: Compilation Customize...

Task	Time
Compile Design	00:00:13
Analysis & Synthesis	00:00:02
Fitter (Place & Route)	00:00:05
Assembler (Generate programming files)	00:00:03
TimeQuest Timing Analysis	00:00:01
EDA Netlist Writer	00:00:02
Program Device (Open Programmer)	

ergasthrio3ask3.bdf

Compilation Report - ergasthrio3ask3

ergasthrio3ask3.bdf

Messages

Type	Message
Success	Quartus II 64-Bit EDA Netlist Writer was successful. 0 errors, 0 warnings
Warning	293000 Quartus II Full Compilation was successful. 0 errors, 14 warnings

System / Processing (101) /

Quartus II 64-Bit - C:/altera/13.0sp1/ergasthrio3ask3/ergasthrio3ask3 - ergasthrio3ask3

File Edit View Project Assignments Processing Tools Window Help

Search altera.com

Project Navigator

Entity	Logic Cells	Dedicated Logic
Cyclone II: EP2C35F672C6	3 (3)	0 (0)
ergasthrio3ask3	3 (3)	0 (0)

ergasthrio3ask3.bdf

Compilation Report - ergasthrio3ask3

Flow Summary

Flow Status	Successful - Sat Nov 07 21:15:38 2020
Quartus II 64-Bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition
Revision Name	ergasthrio3ask3
Top-level Entity Name	ergasthrio3ask3
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	3 / 33,216 (< 1 %)
Total combinational functions	3 / 33,216 (< 1 %)
Dedicated logic registers	0 / 33,216 (0 %)
Total registers	0
Total pins	8 / 475 (2 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)

Tasks

Flow: Compilation Customize...

Task	Time
Compile Design	00:00:12
Analysis & Synthesis	00:00:02
Fitter (Place & Route)	00:00:05
Assembler (Generate programming files)	00:00:02
TimeQuest Timing Analysis	00:00:02
EDA Netlist Writer	00:00:01
Program Device (Open Programmer)	

Messages

System (1) / Processing (101)

Quartus II 64-Bit EDA Netlist Writer was successful. 0 errors, 0 warnings

293000 Quartus II Full Compilation was successful. 0 errors, 14 warnings

351, -19 100% 00:00:12

Πληκτρολογήστε εδώ για αναζήτηση

9:15 μμ 7/11/2020

